

ECSE 323: Digital System Design
Lab #3: g21_stack52, g21_test_bed

Table of Contents

Introduction	2
g21_stack52	3
Circuit Function	3
Circuit Design	4
Registers.....	4
Counter	4
Mode Selection	4
Schematic	6
Simulation and Discussion.....	8
g21_test_bed	10
Circuit Function	10
Circuit Design	11
Single Pulse Generator	11
Stack.....	12
Output Assignments.....	12
Schematic	12
Simulation and Discussion.....	13
Conclusion	14
References	15

List of Figures

Figure 1 g21_stack52 functional block diagram.....	7
Figure 2 g21_stack52 opcode selection circuit schematic	7
Figure 3 Shift register: BUSMUX and LPM_FF pair	8
Figure 4 INIT mode simulation results.....	8
Figure 5 POP mode at ADDR=35 simulation results after INIT operation	9
Figure 6 PUSH mode simulation results.....	9
Figure 7 NOP mode simulation results after PUSH operation	9
Figure 8 RST operation simulation results.....	10
Figure 9 INIT mode with single clock cycle enable signal.....	10
Figure 10 Single pulse generator circuit schematic	12
Figure 11 g21_test_bed circuit schematic	12
Figure 12 g21_test_bed simulation results	13
Figure 13 g21_test_bed SignalTap simulation results	13
Figure 14 Compilation report flow summary for g21_test_bed circuit	14

Introduction

The purpose of this lab was to design a 52 element stack, and implement it on the Altera DE1 board. The stack has four modes of operation: *init*, *pop*, *push*, and *no operation*. It also has an asynchronous reset function. A test bed was designed using a single pulse generator in order to implement the 52-element stack on the Altera board. The SignalTap II logic analyzer and timing simulations were used to validate the circuit. Note that this circuit will become an important building block for the term project which involves playing a card game.

The design was completed using the FPGA design software Quartus. It was also used to compute simulations of the designed circuit. This design was part of the project file *g21_lab3.QPF*.

g21_stack52

Circuit Function

The g21_stack52 circuit has 6 inputs and 4 outputs.

Type	Name	Length (bit)	Purpose
Input	DATA	6	Data to be pushed
Input	MODE	2	Control
Input	ADDR	6	Location to be viewed or popped
Input	ENABLE	1	Enable operations
Input	RST	1	Asynchronous reset
Input	CLK	1	Clock signal
Output	VALUE	6	Value of stack at location specified by ADDR
Output	EMPTY	1	Indicate empty stack
Output	FULL	1	Indicate full stack
Output	NUM	6	Number of stack elements

The circuit has four modes of operation, and an asynchronous reset function.

Operation	Control	Function
NOP	MODE = 00	No operation
INIT	MODE = 01	Initializes registers to 0,1,2,...51
POP	MODE = 10	Returns element at location ADDR, removes it,

		and shifts register values at greater indexes up.
PUSH	MODE = 11	Places DATA element in 0th register and shifts all registers down by one.
RESET	RST = 1	Resets all values of registers to 0.

Circuit Design

The circuit is described in the schematic block diagram design file *g21_stack52.bdf*. The design was implemented in four parts: the registers, the counter, the mode selection, and the reset function.

Registers

The registers are composed of D flip-flops from the LPM library. The *lpm_ff* components were selected as they have several functions which can be used to implement multiple operations [2]. The INIT operation can be completed with the *sset* function with sets registers to pre-assigned values [2]. Both the PUSH and POP operations are performed with the *data_load* and *enable* inputs. The *enable* input is especially useful for the pop operation which only requires the shifting of a certain portion of the stack. Finally, the asynchronous *aclr* function allows the implementation of the reset function.

The capacity to shift values between registers is essential to the function of the stack. A BUSMUX multiplexer is used to link adjoining registers. A control signal is used to select whether values are to be shifted up or down. The output of the multiplexer is fed into the *data_load* input of the *lpm_ff*.

Counter

The counter is used to keep track of the number of registers which are in use. The *lpm_counter* component, from the LPM library, was selected as it offers the option of setting a predetermined value, with *sset*, as well as counting up or down, with *count_en* and *updown* [2]. The EMPTY and FULL signals are determined by comparing the number of registers in use NUM with 0 and 52.

Mode Selection

Each selected operation requires the setting of several signals to control the registers and the counter. For example, the POP operations requires a signal to push the data up, to enable only certain registers, to set the counter to count down, and to enable the counter. To simplify the assignment of such signals, four different opcodes were

created, corresponding to each mode of operation, in the form of constants, with the lpm_constant module [3]. The opcode is a 10 bit value defined below.

Signal	Opcode index	Value			
		NOP	INIT	PUSH	POP
data_select	9	0	0	0	1
sset	8	0	1	0	0
count_en	7	0	0	1	1
updown	6	0	0	1	0
ADDR	5..0	110100 (52)	000000	000000	000000

The signals functions are defined below.

Signal	Function
data_select	Select data to be pushed up or down into the registers during the POP or PUSH operations.
sset	Set the registers and the counter to their predetermined values for the INIT operation.
count_en	Enables counting for the POP or PUSH operations.
updown	Determines if the counter counts up or down.
ADDR	Used in conjunction with the g21_pop_enable circuit to determine the enable signal.

The g21_pop_enable circuit was designed in lab 2 and is used to assign the enable signal for every operation. The use of the same components for each mode of operation facilitates timing considerations which are quite relevant as discussed further. For the modes which require all the registers be enabled, INIT and PUSH, the address passed to the circuit is 000000 which returns all 52 signals high. For the no operation mode, none of the registers are enabled by passing the address 110100 (52) to the pop enable

circuit which returns all 52 signals low. Finally, the address specified by the ADDR input replaces the opcode in its place for the pop operation.

As mentioned above, the use of the g21_pop_enable circuit to produce the array of enable signals for every operation facilitates timing considerations. The g21_pop_enable circuit employs ROM and it clock enabled. This causes the enable circuit to have an additional delay of 1 clock cycle. This becomes increasingly relevant when the enable signal is a single clock-cycle in length. In particular, it was found that the INIT operation was not occurring despite it being the selected mode, because the sset input was activated before the *enable* input was active as it did not clock dependant. The one clock-cycle delay meant that the INIT operation could not take place. To solve this issue, extra flip-flops were implemented with the opcode elements which interacted with the registers. The flip-flops, being clock-enabled as well, solved this issue. Simulations showed that the enable signal was actually 2 clock-cycles long. Consequently, two flip-flops are used to delay the rest of the opcode signals.

Depending on the selected mode, several conditions need to be checked within the circuit before executed the operation. For example, a PUSH operation can only take place if the MODE control bits are set to 10, the stack if not full, and the enable signal is on. A series of multiplexers are used to check conditions for each operation to take place. When a condition is not met, the no operation opcode is passed through.

Schematic

Since the schematic of the stack is very large and complex, it is not shown in its entirety in this report. Rather, a block diagram is shown, as well as the mode selection circuit and an instance of the BUSMUX and lpm_ff pair which constitutes a shift register. For a view of the full schematic diagram, please refer to design file *g21_stack52.bdf*.

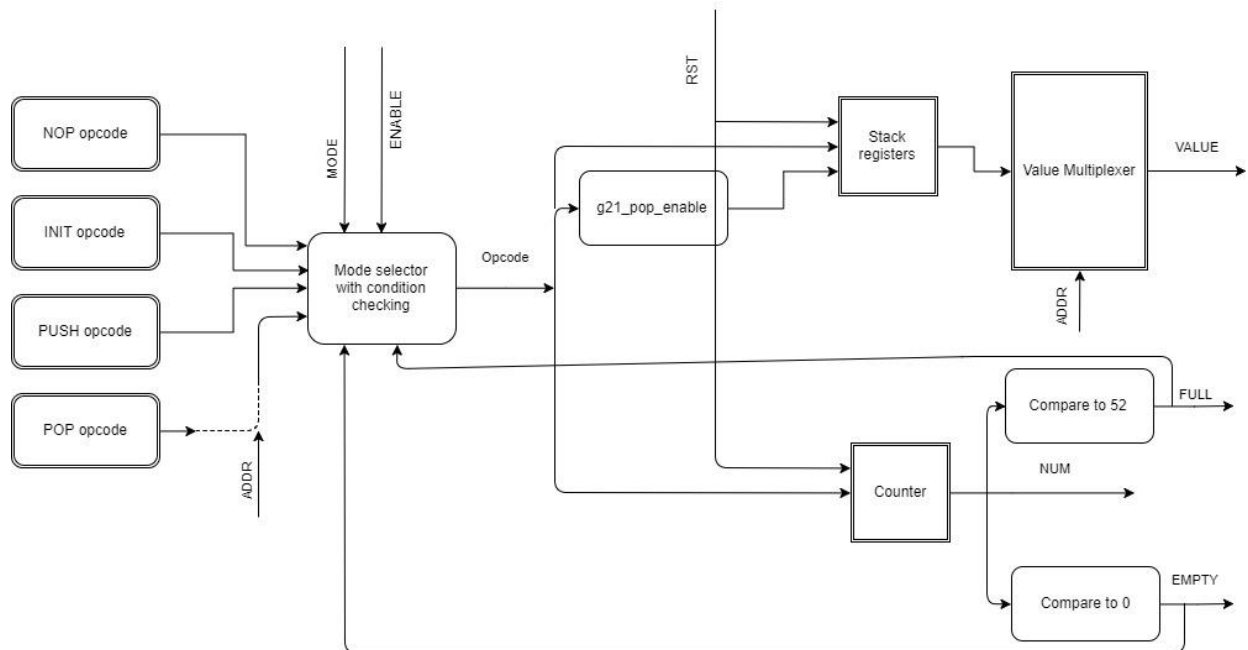


Figure 1 g21_stack52 functional block diagram

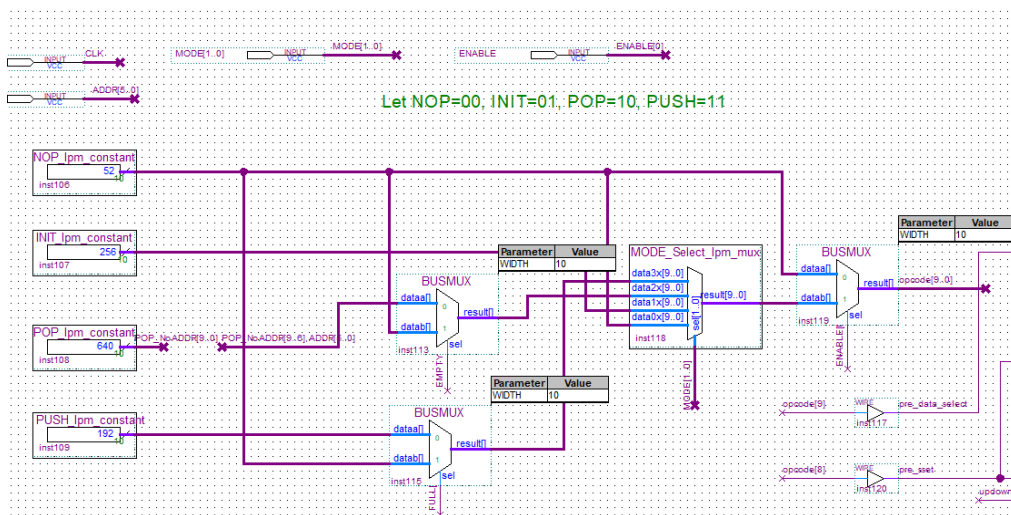


Figure 2 g21_stack52 opcode selection circuit schematic

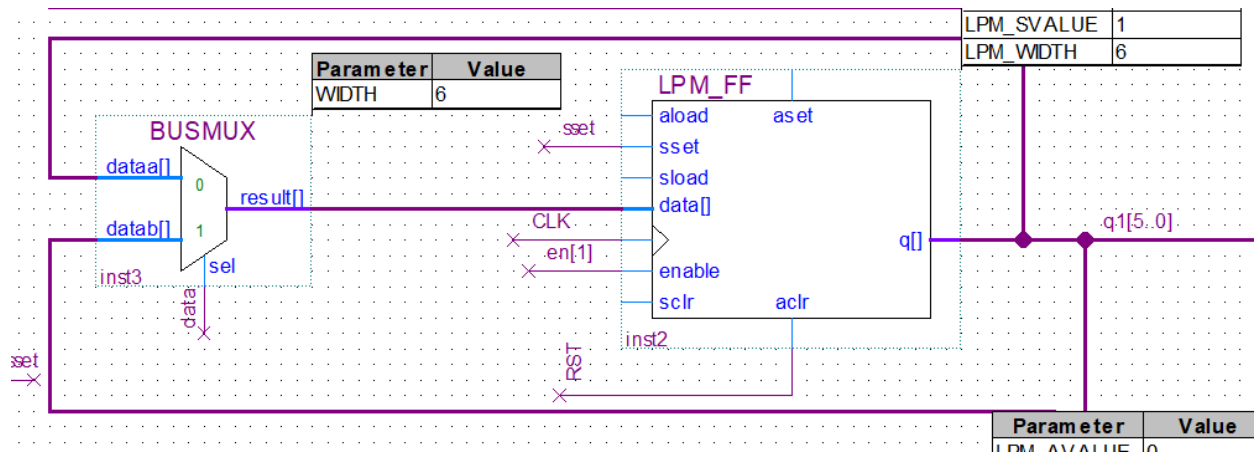


Figure 3 Shift register: BUSMUX and LPM_FF pair

Simulation and Discussion

Timing simulations were done on the circuit to ensure it was functioning correctly. Tests were done using the simulation file *g21_stack52.vwf* on all four modes of operation plus the reset function. It should be noted that simulations using a constant enable signal can be misleading as it can mask timing issues as it was our case. It is important in simulations, to use waveforms which are representative of the physical signals which will be passed to the signal. As it is seen in the *g21_test_bed* circuit, *g21_stack52* circuit is to be used with enable signals which lasted a single clock cycle. This such simulation it is important to simulate it as such as well. This can be seen in Figure 9 INIT mode with single clock cycle enable signal. It should be noted that the maximum propagation delay is 19.104 nanoseconds. This indicates the maximum operational frequency of the clock is 52 MHz. Below are snapshots of the simulation results for INIT, POP, PUSH, NOP and RST:

 


Figure 4 INIT mode simulation results

 


Figure 5 POP mode at ADDR=35 simulation results after INIT operation

 


Figure 6 PUSH mode simulation results

 


Figure 7 NOP mode simulation results after PUSH operation

 


Figure 8 RST operation simulation results

 


Figure 9 INIT mode with single clock cycle enable signal

g21_test_bed

Circuit Function

The test-bed circuit has 5 inputs and 6 outputs. It is used to implement the g21_stack52 circuit on the physical Altera DE1 board.

Type	Name	Length (bit)	Purpose
Input	CLK	1	Clock Signal
Input	pushButton	1	Input mapped to a button on the board and triggers a single enable pulse
Input	RSTButton	1	Input mapped to a button on the board and triggers the reset function

Input	dipswitch2	6	Input mapped to 6 switches on the board and defines the value of ADDR
Input	dipswitch1	2	Input mapped to 2 switches on the board and defines the value of MODE
Output	LEDmod	7	7-segment code for mod13 of VALUE
Output	LEDfloor	7	7-segment code for floor of VALUE
Output	FULL*	1	Output mapped to a green LED on the board and triggers when the stack is full
Output	EMPTY*	1	Output mapped to a red LED on the board and triggers when the stack is empty

*Note that the FULL and EMPTY outputs were not required in the lab instructions [1] but they were added to make testing on the board easier.

Circuit Design

The g21_test_bed circuit is used to implement the g21_stack52 circuit on the physical board. To do so, the circuit is comprised of three parts: receive input from user, process information, show result to user. First, the circuit receives information from the user by assigning inputs to appropriate pins on the board. Additionally, a single pulse generator circuit is implemented with the enable signal as to ensure the inherent mechanical “bouncing” of the switch does not cause create noise in the enable signal. Second, the circuit performs its operation based on the input with the g21_stack52 circuit. Finally, the output is shown the user by lighting the correct LEDs available on the board.

Single Pulse Generator

The single pulse generator functions as a gate for the enable signal. The enable signal can only be high for one clock cycle every 20 ms. This prevents several pulses going through the circuit which could cause the circuit to push a value 2-3 times instead of once. As seen in the Figure 10 Single pulse generator circuit schematic, the circuit is implemented with a counter. Once the enable signal is high, the counting begins. While the value of the counter is between 1 and 20000000, the register which holds the enable signal is cleared and the counting is enabled. Once the required time has elapsed, another enable pulse may be passed to the rest of the circuit.

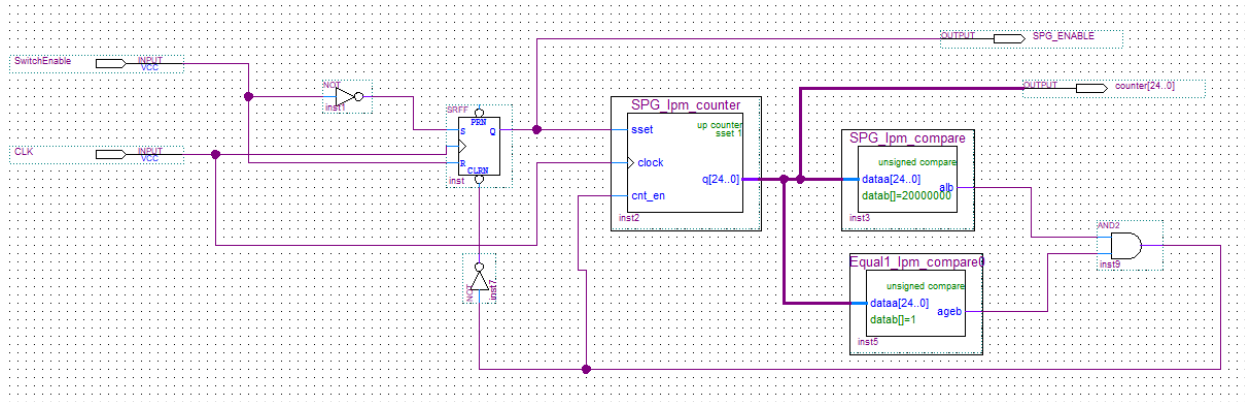


Figure 10 Single pulse generator circuit schematic

Stack

This is an instance of the stack52 circuit that was described in the **g21_stack52** section of this report.

Output Assignments

The outputs are shown to the user by lighting different combinations of LEDs. The FULL and EMPTY outputs are displayed by lighting a green and a red LED. The VALUE is more complicated to display as it is a 6-bit integer. Circuits which were developed in earlier labs are used.

The g21_Modulo13 circuit from Lab #1 is used to separate the VALUE into the mod13 and its floor. The user can recover the VALUE by multiplying floor by 13 and adding mod13. Each of these values is presented on a 7 segments LED display. The g21_7_segment_decoder from Lab #2 is used to properly map values to the correct pin assignments.

Schematic

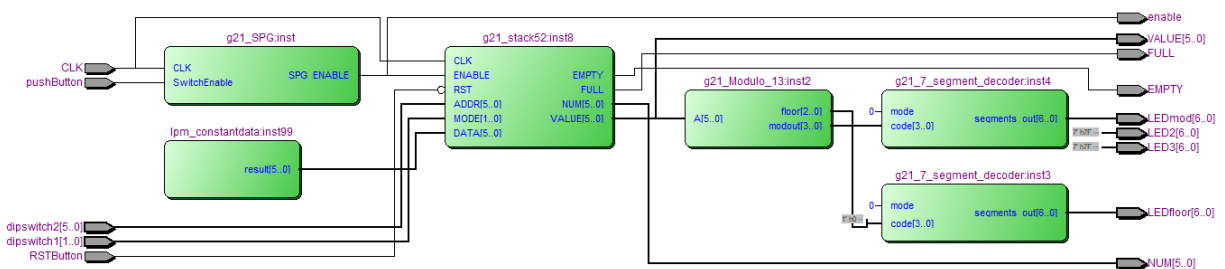


Figure 11 g21_test_bed circuit schematic

*Note that the outputs enable, VALUE and NUM are not described in the Circuit Function because they were only used for debugging purposes. Similarly, LED2 and LED3 are not actual outputs, they simply set the two unused 7-segment displays to be off.

Simulation and Discussion

Timing simulations were done on the circuit to ensure it was functioning correctly. The results of the simulation can be found in Figure 12 g21_test_bed simulation results. Tests were done using the simulation file *g21_test_bed_tim.vwf* on all four modes of operation plus the reset function. Below is a snapshot of the simulation results for INIT. Other modes are not shown as they were already tested for stack52 and the goal of this simulation is to show that the test-bed works as a whole:

 


Figure 12 g21_test_bed simulation results

From the TimeQuest timing analyzer, it was determined that the longest propagation delay in the circuit was 25.839ns. This means the minimum clock frequency should allow for this delay. The associated maximum frequency is 38.7 MHz.

A SignalTap simulation was also conducted to ensure that the circuit was functional on the DE1 board and not only when doing regular timing simulations. Here is a snapshot of the SignalTap results when ADDR (dipswitch2) = 4 and MODE (dipswitch1) = INIT:

 


Figure 13 g21_test_bed SignalTap simulation results

Furthermore, a summary of resource utilization was extracted from the compilation flow summary. From it, information can be analyzed about the number of logic elements registers and pins that are used by the circuit on the DE1 board:

Flow Summary	
Flow Status	Successful - Tue Nov 07 14:21:42 2017
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	g21_lab3
Top-level Entity Name	g21_test_bed
Family	Cyclone II
Device	EP2C20F484C7
Timing Models	Final
Total logic elements	1,353 / 18,752 (7 %)
Total combinational functions	1,055 / 18,752 (6 %)
Dedicated logic registers	911 / 18,752 (5 %)
Total registers	911
Total pins	54 / 315 (17 %)
Total virtual pins	0
Total memory bits	6,144 / 239,616 (3 %)
Embedded Multiplier 9-bit elements	0 / 52 (0 %)
Total PLLs	0 / 4 (0 %)

Figure 14 Compilation report flow summary for g21_test_bed circuit

Conclusion

The g21_stack52 circuit was designed and implemented on the Cyclone II Altera DE board by using a test bed which implemented a single pulse generator. It is important to consider the application of a circuit when simulating it to ensure it functions correctly, as seen with the stack circuit timing issues. Circuits which use the stack component should have a clock frequency inferior to 52 MHz (which is fine since the DE1 board operates at 50 MHz) to account for the propagations delays.

References

- [1] Prof. J. Clark, Lab Instructions, "ECSE-323 Digital Systems Design: Lab #3 - Sequential Circuit Design", Department of Electrical and Computer Engineering, McGill University, Oct. 2017.

- [2] *LPM Quick Reference Guide*. Altera Corporation, 1996, pp. 26-28.

- [3] "Opcode definition by The Linux Information Project (LINFO)", *Linfo.org*, 2017. [Online]. Available: <http://www.linfo.org/opcode.html>. [Accessed: 03- Nov- 2017].